

Continuous Assessment Test(CAT) – II OCT 2024


Programme	:	B.Tech (ECE/ECM)	Semester	:	Fall Semester 2023-24
Course Code & Course Title	:	Sensors Technology	Code	:	BECE409E
Faculty	:	Dr. MANIMARAN.P	Class Nbr	:	CH2024250100166
Duration	:	90 Mins	Slot	:	A1

General Instructions:

- Write only your registration number on the question paper in the box provided and do not write other information.
- Use statistical tables supplied from the exam cell as necessary
- Use graph sheets supplied from the exam cell as necessary
- Only non-programmable calculator without storage is permitted

Answer all questions

Q. No	Sub Sec.	Description	Marks	Blooms Taxonomy Level
1.		In a low-voltage Schering bridge designed for the measurement of permittivity, the branch ab consists of two electrodes between which the specimen under test may be inserted; arm bc is a non-reactive resistor R_3 in parallel with a standard capacitor C , arm cd is a non-reactive resistor R_4 in parallel with a standard capacitor C_4 ; arm da is a standard air capacitor of capacitance C_2 . Without the specimen between the electrodes, balance is obtained with the following values; $C_3=C_4 = 100 \text{ pF}$, $C_2 = 120 \text{ pF}$, $R_3 = R_4 = 6000 \text{ Ohms}$. With the specimen inserted these values become $C_3 = 150 \text{ pF}$, $C_4 = 2000 \text{ pF}$, and $R_3 = R_4 = 7000 \text{ Ohms}$. In each test $\omega = 4000 \text{ rad/s}$. Find the relative permittivity of the specimen.	10	K4
2.	i) ii) iii)	A Kelvin double bridge (shown in Fig) each of the ratio arms $P = Q = p = q = 2000 \text{ Ohms}$. The emf of the battery is 100 V and a resistance of 5 Ohms is included in the battery circuit. The galvanometer has a resistance of 400 Ohms and the resistance of the link connecting the unknown resistance to the standard resistance may be neglected. The bridge is balanced when the standard resistance $S = 0.002 \text{ Ohms}$. Determine the value of unknown resistance. (3 Marks) Determine the current (approximate value) through the unknown resistance R at balance. (2 Marks) Determine the deflection of the galvanometer when the unknown resistance, R , is changed by 0.1 percent from its value at balance. The galvanometer has a sensitivity of $100 \text{ mm}/\mu\text{A}$. (5 Marks)	10	K5

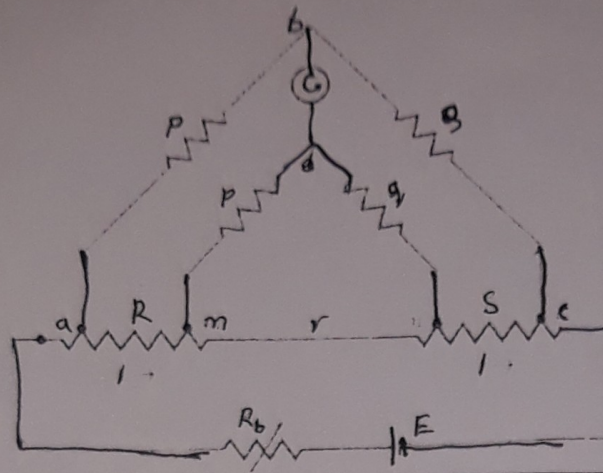

3.		<p>Design an integrator circuit using an operational amplifier (Op-Amp) that satisfies the following specifications:</p> <ul style="list-style-type: none"> The input signal is a sine wave with peak amplitude of 1 V and a frequency of 1 kHz. The integrator should output a triangular wave with peak amplitude of 5 V. Use a power supply of ± 12 V for the Op-Amp. 	10	K4
4.		<p>With the increasing demand for compact and highly sensitive MEMS and NEMS sensors, how do different micromachining techniques (such as bulk micromachining, surface micromachining, and high-aspect-ratio micromachining) affect the structural integrity and operational efficiency of these sensors? Provide examples of specific sensor applications that have benefited from advanced micromachining methods.</p>	10	K2
5.	<p>i) Using a healthcare facility as a case study, evaluate how IIoT can be utilized to enhance patient monitoring, improve workflow automation, and reduce errors in medical procedures. (5 Marks)</p> <p>ii) Examine a real-life example of an IIoT deployment in healthcare (e.g., remote patient monitoring, smart hospital rooms). Highlight the benefits and challenges encountered during implementation. (5 Marks)</p>	<p>In modern healthcare, IoT-enabled devices and sensors have the potential to transform patient care, making monitoring and diagnostics more real-time, personalized, and efficient. However, there are still challenges in deploying Industrial IoT (IIoT) solutions at scale in healthcare due to concerns around data privacy, infrastructure costs, and integration with existing systems.</p>	10	K6